

**15ECE381 Circuits and Communication Laboratory /****15ECE383 Linear Integrated Circuits Laboratory****B. Tech (ECE and EIE) – V Semester****Experiment 5****Schmitt Trigger****NAME** : B SUMANTH**ROLL NO** : CB.EN.U4ECE18211**SECTION** : ECE-C**GROUP** : C2**AIM:**

To design a circuit to implement the given VTC curve using an Op-Amp. This is basically to design a Schmitt Trigger based on the given threshold values.

**Instructions:**

1. All resistors used in your design should be from the E24 series
2. You may make use power supplies of  $\pm 10$  V.
3. Please ensure proper polarity for the connections to the power supply pins (4 and 7) of the opamp. Wrong polarity may cause the opamp to explode.


**Questions:**


1. Design and implement a circuit to obtain the following transfer characteristics with

$$V_{UT}, V_{LT} = \{2.5, -1.5\}$$

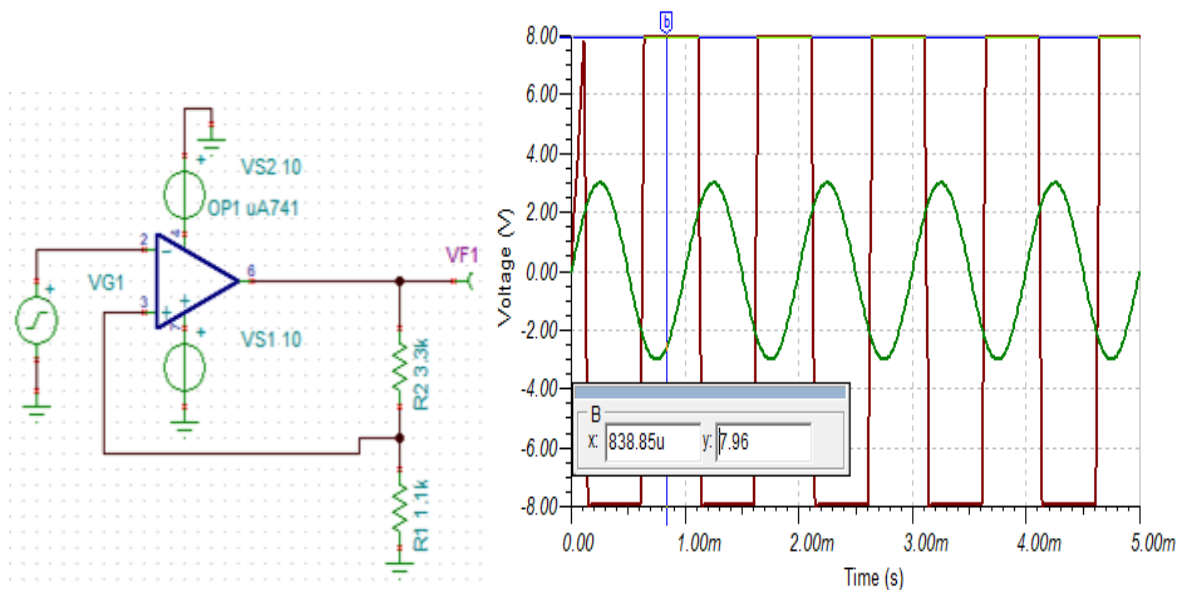**ANS:**

We have taken Saturation Voltage as 8volts ( 8volts is taken from simulation)



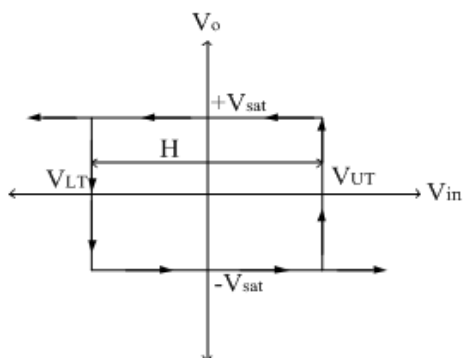

Design :

Given

$$V_{UT} = 2.5V$$

$$V_{LT} = -1.5V$$

OKT,

$$V_{UT} = \frac{R_1}{R_1 + R_2} V_{sat} + \frac{R_2}{R_1 + R_2} V \quad \text{--- (1)}$$

$$V_{LT} = \frac{-R_1}{R_1 + R_2} V_{sat} + \frac{R_2}{R_1 + R_2} V \quad \text{--- (2)}$$

① - ②

$$V_{UT} - V_{LT} = \frac{2R_1}{R_1 + R_2} V_{sat}$$

$$V_{sat} = 8V \text{ (taken from simulation)}$$

$$2.5 - (-1.5) = \frac{2R_1}{R_1 + R_2} (8)$$

$$4 = \frac{16R_1}{R_1 + R_2} \Rightarrow R_1 + R_2 = 4R_1 \Rightarrow \boxed{R_2 = 3R_1}$$

as from the E24 series,




$$\boxed{R_1 = 1.1K \text{ ohms}}$$

$$\boxed{R_2 = 3.3K \text{ ohms}} \quad \text{--- (3)}$$

Now, (3) in (1)


$$2.5 = \frac{1K}{1K + 3K} (8) + \frac{R_2}{R_1 + 3R_1} V = \frac{1K(8)}{4R_1} + \frac{R_2}{4R_1} V$$

$$2.5 = \frac{8}{4} + \left(\frac{3}{4}\right)V \Rightarrow 2 = 3V \Rightarrow \boxed{V = \frac{2}{3} = 0.67V}$$

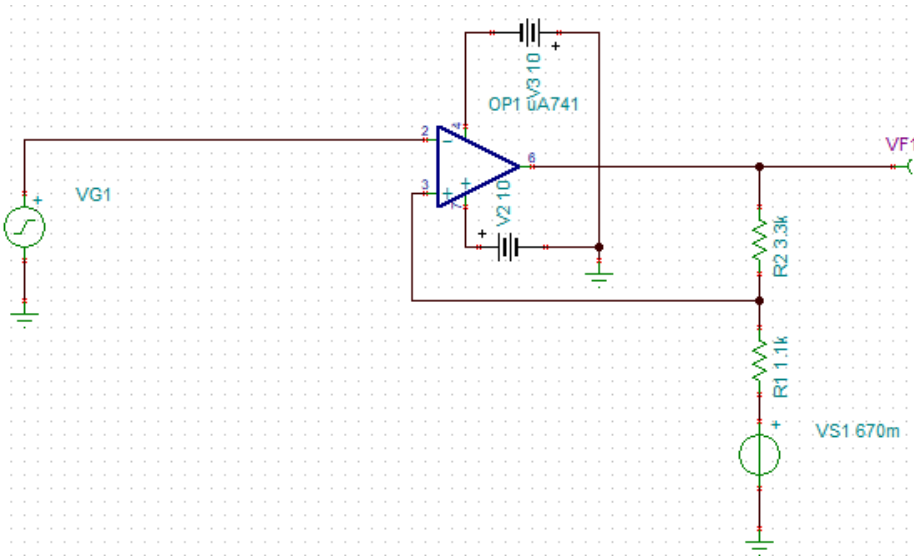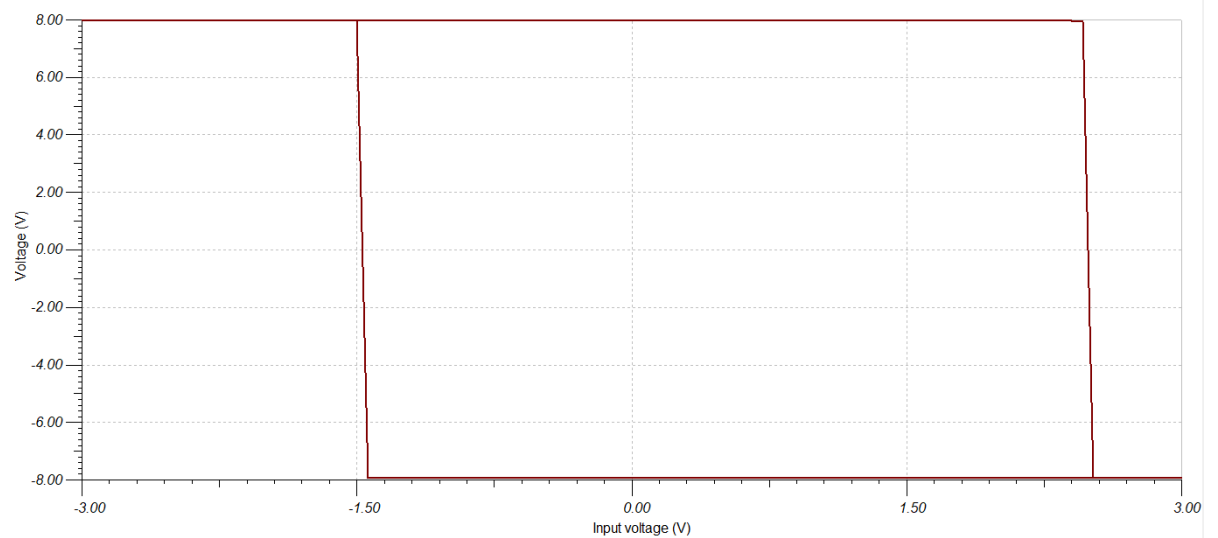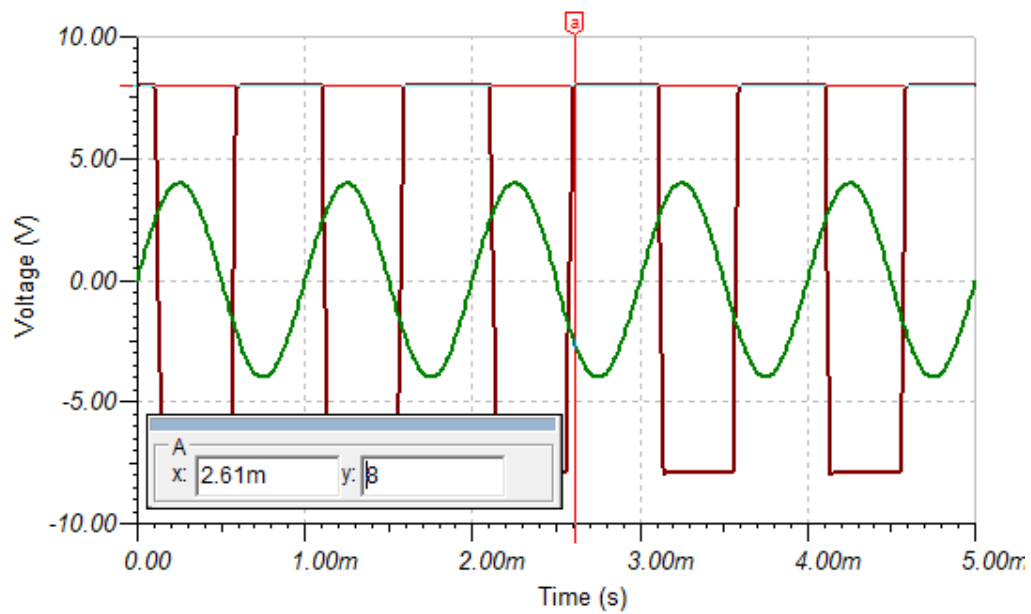
**Circuit:****Working:**

2. Plot the input and output waveforms for input amplitudes of approximately 5 V, 250 mV,  $V_{UT}$ , and  $V_{LT}$  with freq. of 1 KHz.


### $V_i=5\text{Volts}$

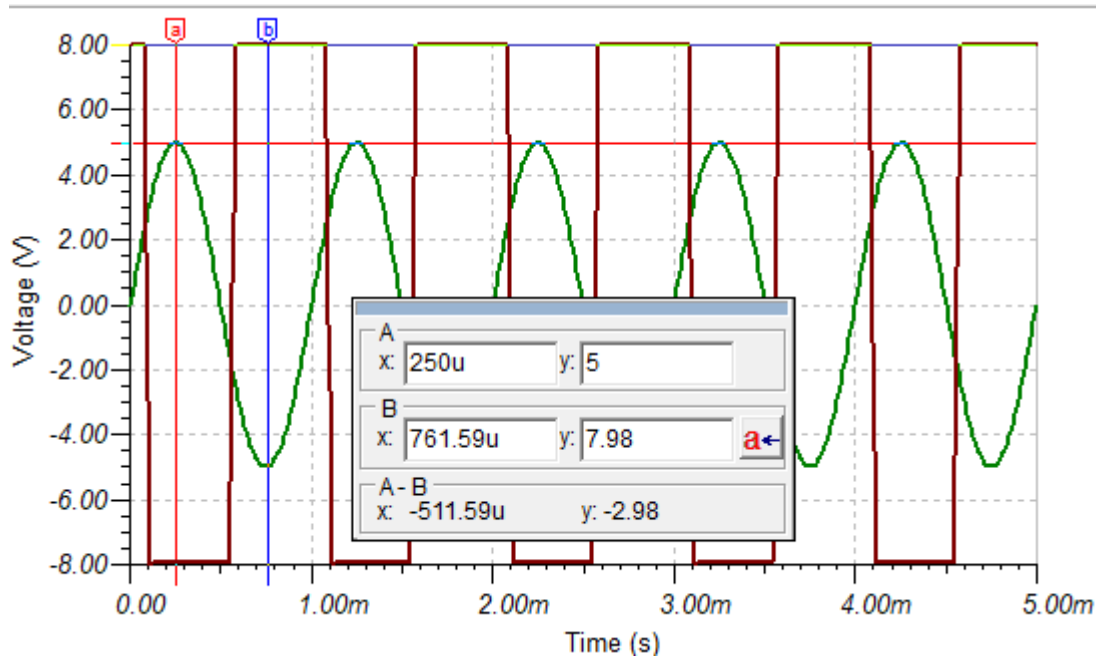


### $V_i=250\text{mVolts}$

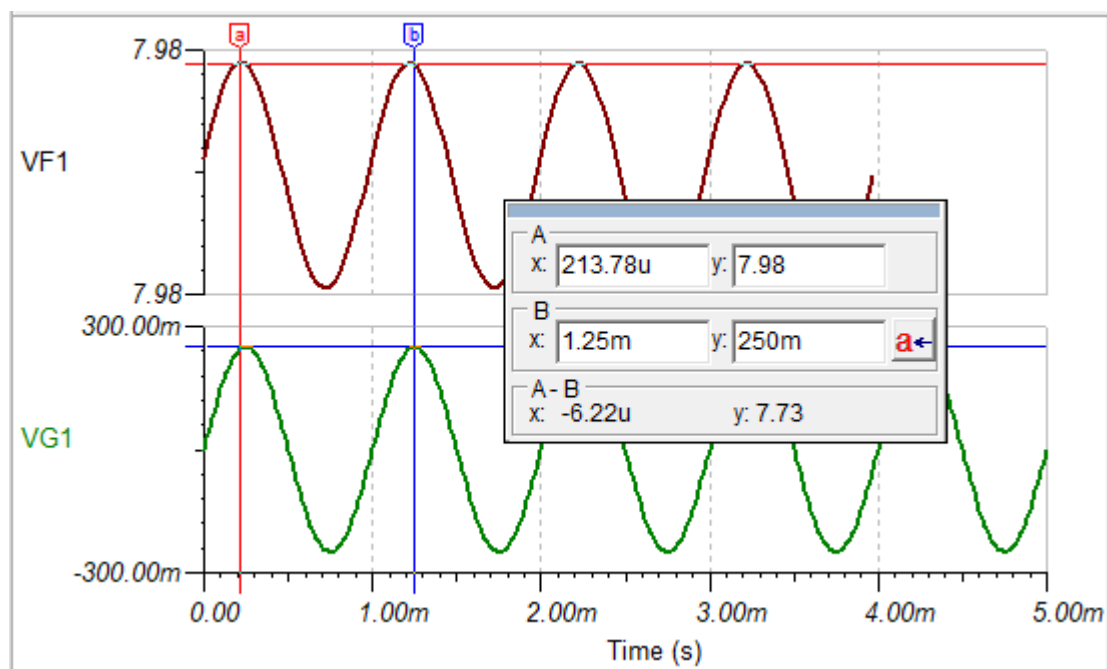

$V_i = V_{UT} = 2.5$  Volts

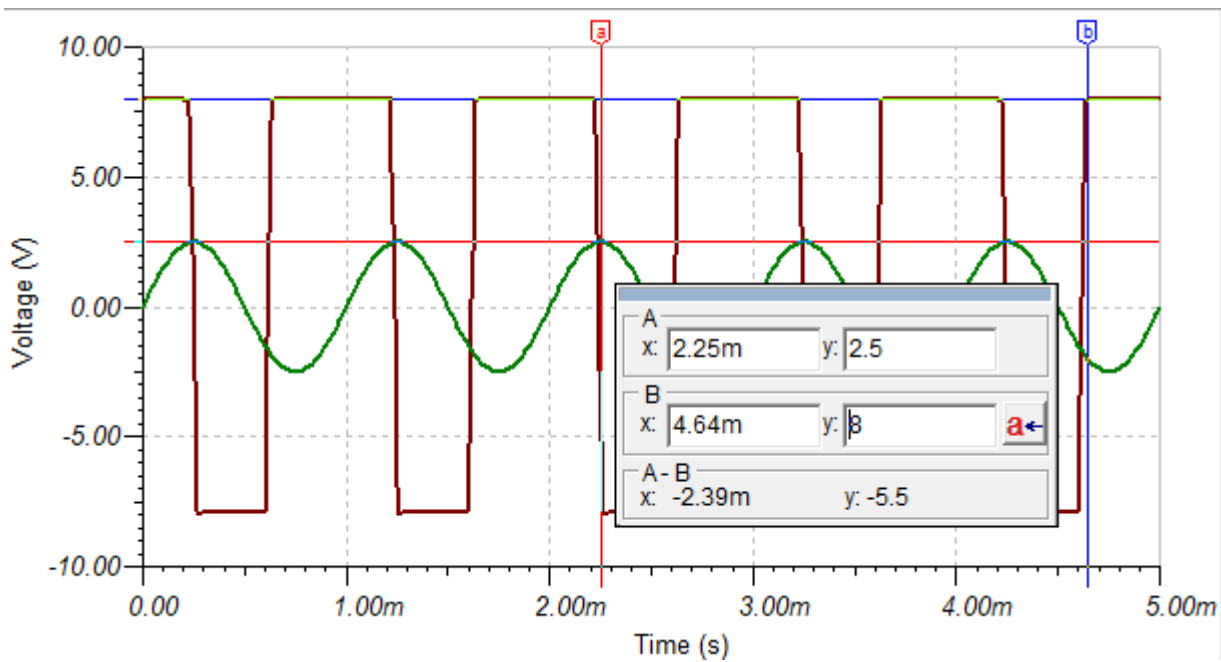

$V_i = V_{LT} = -1.5$  Volts

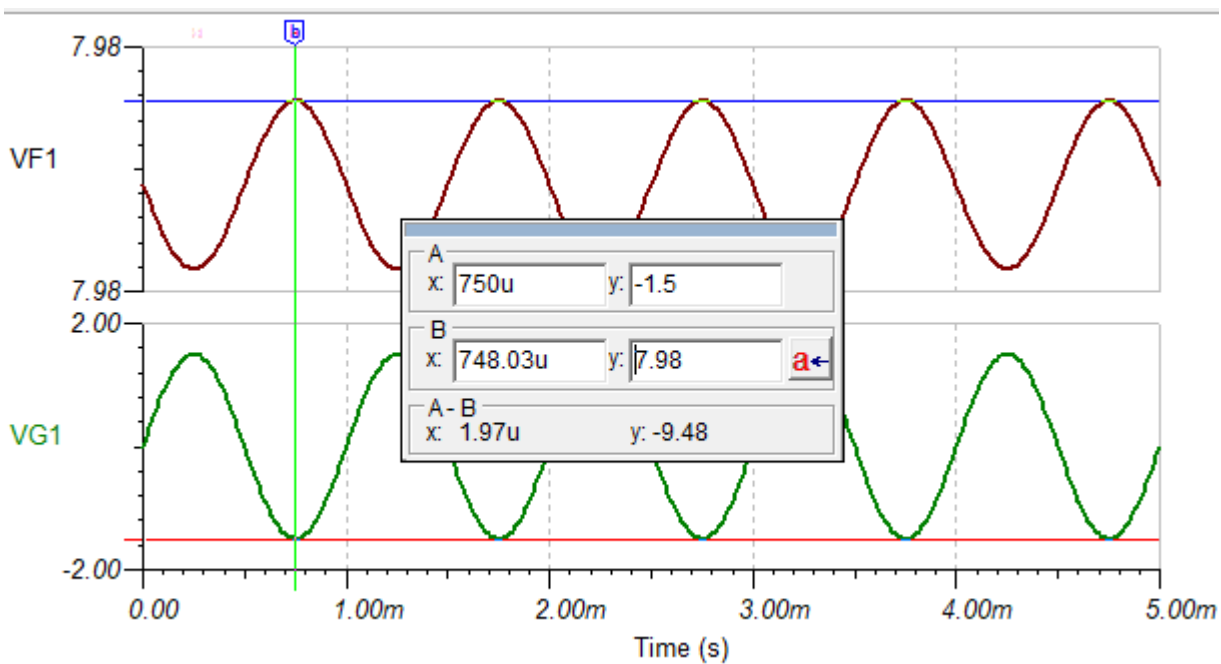

3. Determine the hysteresis width of the designed circuit. What is the purpose of providing hysteresis width?

Ans:


From the graph we noted that

$V_{UT} = 2.5$

$V_{LT} = -1.5$

We know that,

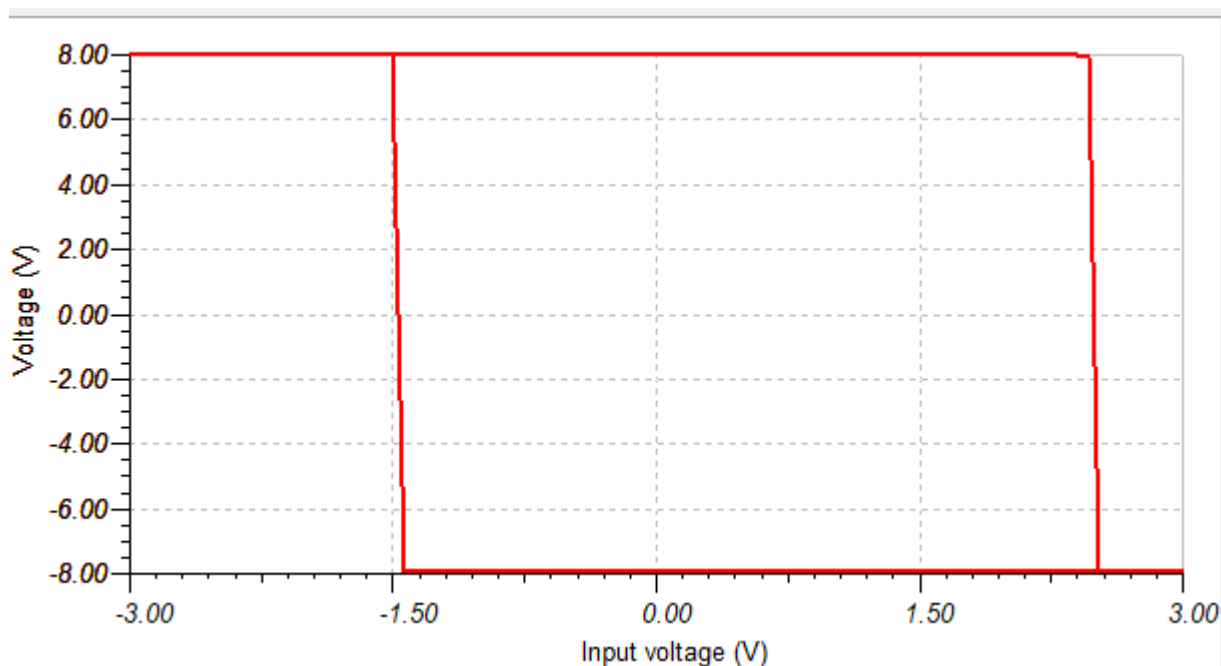Hysteresis width =  $V_{UT} - V_{LT} = 2.5 - (-1.5) = 2.5 + 1.5 = 4$




Hysteresis width=4Volts

#### Inference Questions:

- For the given circuits, calculate the upper and lower threshold voltages and the hysteresis width.

Schmitt trigger with zero-reference

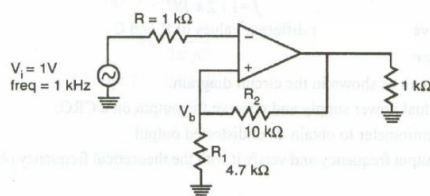

$$(1) R_1 = 4.7k\Omega \quad R_2 = 10k\Omega$$

$$V_{OT} = \frac{R_1}{R_1 + R_2} (V_{sat})$$

$$= \frac{4.7k}{14.7k} (8)$$

$$= 2.6V$$

$$V_{LT} = -2.6V$$


WKT

$$\text{hysteresis width} = V_{OT} - V_{LT}$$



$$= 2.6 - (-2.6)$$

$$= 5.2V$$
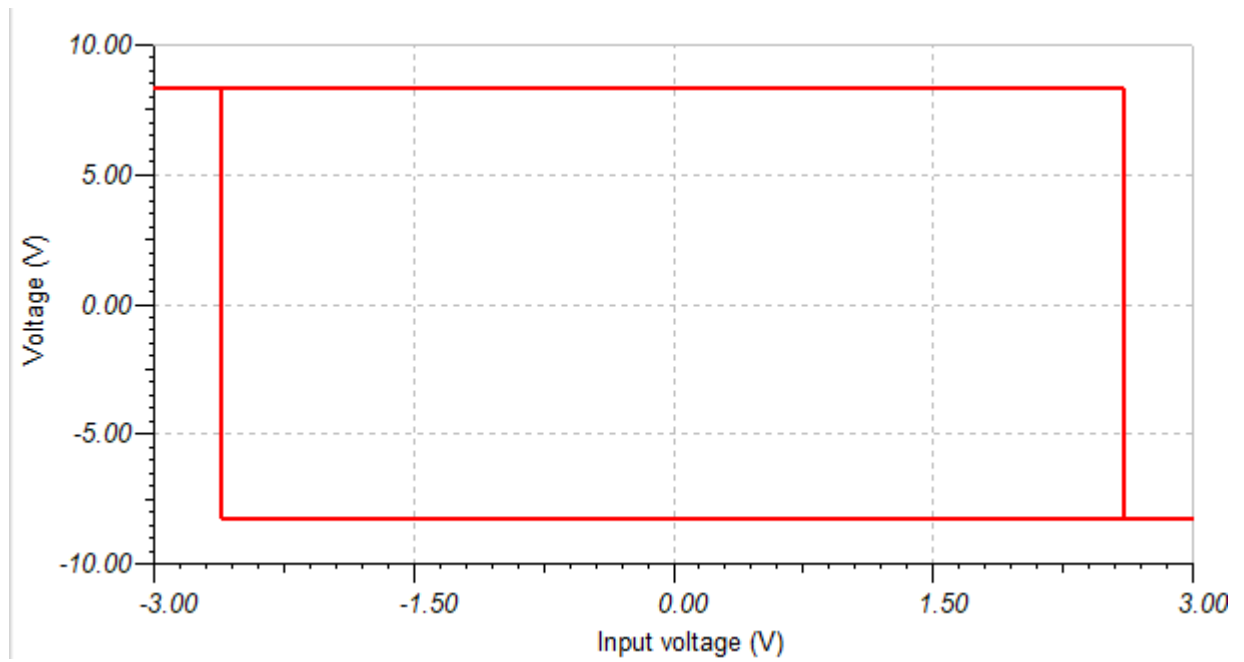
$$\therefore \text{Hysteresis width} = \underline{5.2V}$$




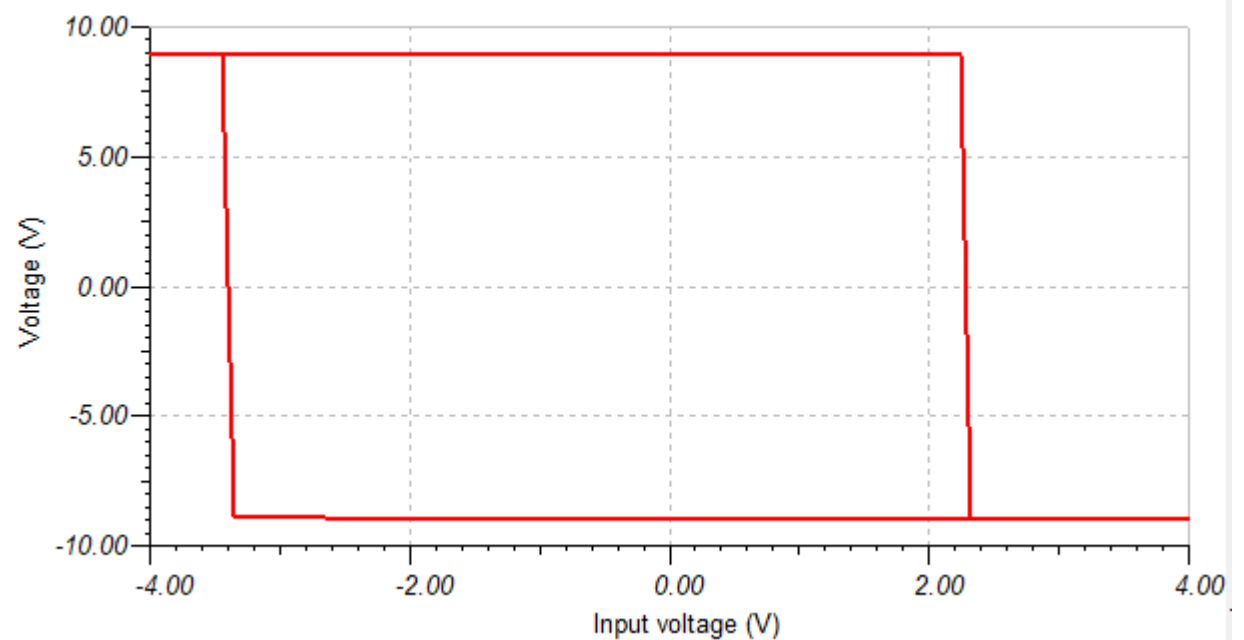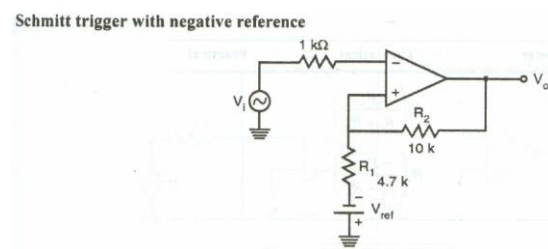We got upper and lower threshold voltages are same because of **SYMMETRIC CIRCUIT**



Here upper and lower threshold voltages are 2.3V and -3.4V. So **hysteresis width is 5.7Volts**

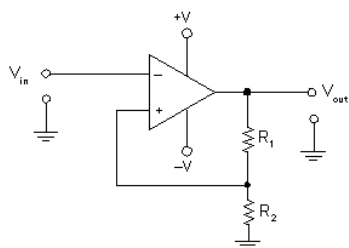2. Design the circuit below to obtain a hysteresis width of 3 V with an UTP of = 2 V?



$$V_{UT} = \left( \frac{R_1}{R_1 + R_2} \right) V_o + \left( \frac{R_2}{R_1 + R_2} \right) V_{ref}$$

$$V_{LT} = -\left( \frac{R_1}{R_1 + R_2} \right) V_o + \left( \frac{R_2}{R_1 + R_2} \right) V_{ref}$$

$$V_{UT} - V_{LT} = 3 \quad V_o = \pm V_{sat}$$

$$3 = \left( \frac{2R_1}{R_1 + R_2} \right) 8 \Rightarrow \frac{R_1 + R_2}{R_1} = \frac{16}{3}$$

$$\Rightarrow R_1 + R_2 = 5.34 R_1$$

$$R_2 = 4.34 R_1$$

$$R_1 = 1.2 \text{ k}\Omega, \quad R_2 = 5.2 \text{ k}\Omega$$

$$\Rightarrow 2 = \left( \frac{R_1}{5.34 R_1} \right) 8 + \left( \frac{4.34 R_1}{5.34 R_1} \right) V_{ref}$$

$$\Rightarrow 2 = \frac{8}{5.34} + \frac{4.34}{5.34} V_{ref}$$

$$\Rightarrow \boxed{V_{ref} = 0.62 \text{ V}}$$